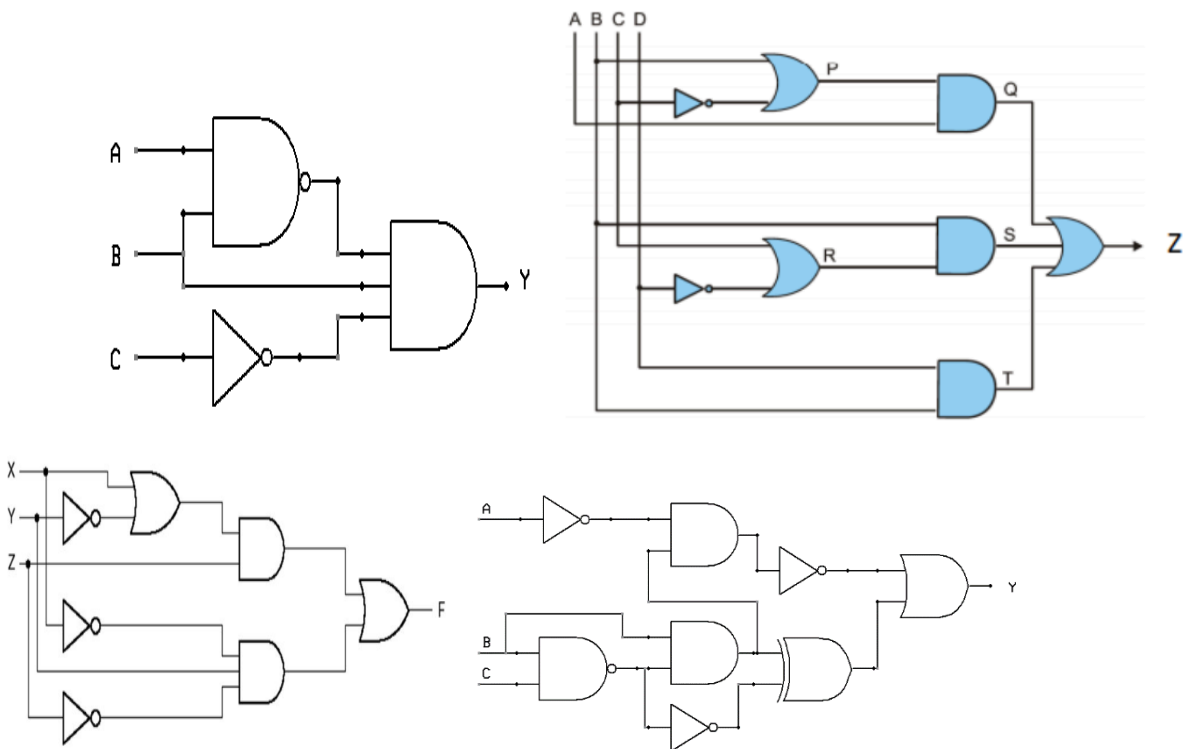


Course Code: EE1005	Course Name: Digital Logic Design (DLD)
Instructor Name:	Muhammad Rahim
Date of Submission	23 rd March, 2025

- Write the Boolean expressions for the following logic circuits and simplify these expressions using Boolean algebra.



- Consider the given expression, and simplify it using Boolean algebra. Also, develop the truth table and circuit of simplified form.

$$\bar{A}BC + A\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}C + ABC$$

- Draw the circuit diagram of the following expression using NAND only, NOR only Gates
(i) $A'B + B'A$ (ii) $A'B' + AB$
- Draw the circuit Diagram of the following expressions using (Dual Symbols) NAND with Negative-OR (i) $(AB + C')(DE + F')$ (ii) $(A' + B)(C + D')(E + F)$
- Implement the following Boolean function F, using the two-level forms:

(a) AND-NOR, (b) OR-NAND (c) NAND –NAND (d) NOR_NOR logic diagrams
 $F(A, B, C, D) = \Sigma(0,1,2,8,9,12)$; $d(A, B, C, D) = \Sigma(3, 4, 10,11)$

6. Design a combinational circuit with three inputs and one output. The output is equal to logic 1 when the binary value of the input is less than 3 AND the output is logic 0 otherwise.

7. Using a Karnaugh map convert the standard POS expression

$$(\overline{A} + \overline{B} + C + D)(A + \overline{B} + C + D)(A + B + C + \overline{D})(A + B + \overline{C} + \overline{D})(\overline{A} + B + C + \overline{D})(A + B + \overline{C} + D)$$

into a:

- (i) Minimum POS expression (ii) Standard SOP expression
 (iii) Minimum SOP expression

8. Use a Karnaugh map to find the minimum POS for each expression:

(a) $(A + B + C)(\overline{A} + \overline{B} + \overline{C})(A + \overline{B} + C)$

(b) $(X + \overline{Y})(\overline{X} + Z)(X + \overline{Y} + \overline{Z})(\overline{X} + \overline{Y} + Z)$

9. Convert each of the following POS expressions to minimum SOP expressions using a Karnaugh map:

(a) $(A + \overline{B})(A + \overline{C})(\overline{A} + \overline{B} + C)$

(b) $(\overline{A} + B)(\overline{A} + \overline{B} + \overline{C})(B + \overline{C} + D)(A + \overline{B} + C + \overline{D})$

10. Simplify the following Boolean function F together with the don't-care conditions d; then express the simplified function in minimum SOP and minimum POS.

(a) $F(A, B, C, D) = \Sigma(0,6,8, 13, 14)$; $d(A, B, C, D) = \Sigma(2, 4, 10)$

(b) $F(A, B, C, D) = \Sigma(1, 3, 5, 7, 9,15)$; $d(A, B, C, D) = \Sigma(4, 6, 12, 13)$